

6 Op-Amp Basics

The operational amplifier is one of the most useful and important components of analog electronics. They are widely used in popular electronics. Their primary limitation is that they are not especially fast: The typical performance degrades rapidly for frequencies greater than about 1 MHz, although some models are designed specifically to handle higher frequencies.

The primary use of op-amps in amplifier and related circuits is closely connected to the concept of negative feedback. Feedback represents a vast and interesting topic in itself. We will discuss it in rudimentary terms a bit later. However, it is possible to get a feeling for the two primary types of amplifier circuits, inverting and non-inverting, by simply postulating a few simple rules (the “golden rules”). We will start in this way, and then go back to understand their origin in terms of feedback.

6.1 The Golden Rules

The op-amp is in essence a differential amplifier of the type we discussed in Section 5.7 with the refinements we discussed (current source load, follower output stage), plus more, all nicely debugged, characterized, and packaged for use. Examples are the 741 and 411 models which we use in lab. These two differ most significantly in that the 411 uses JFET transistors at the inputs in order to achieve a very large input impedance ($Z_{in} \sim 10^9 \Omega$), whereas the 741 is an all-bipolar design ($Z_{in} \sim 10^6 \Omega$).

The other important fact about op-amps is that their *open-loop gain* is huge. This is the gain that would be measured from a configuration like Fig. 29, in which there is no feedback loop from output back to input. A typical open-loop voltage gain is $\sim 10^4$ – 10^5 . By using negative feedback, we throw most of that away! We will soon discuss why, however, this might actually be a smart thing to do.

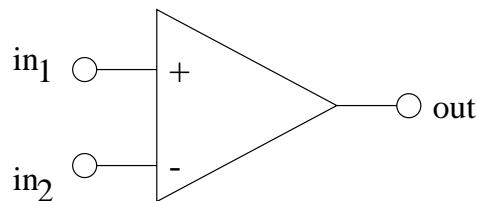


Figure 29: Operational amplifier.

The golden rules are idealizations of op-amp behavior, but are nevertheless very useful for describing overall performance. They are applicable whenever op-amps are configured with negative feedback, as in the two amplifier circuits discussed below. These rules consist of the following two statements:

1. The voltage difference between the inputs, $V_+ - V_-$, is zero.
(Negative feedback will ensure that this is the case.)

2. The inputs draw no current.

(This is true in the approximation that the Z_{in} of the op-amp is much larger than any other current path available to the inputs.)

When we assume ideal op-amp behavior, it means that we consider the golden rules to be exact. We now use these rules to analyze the two most common op-amp configurations.

6.2 Inverting Amplifier

The inverting amplifier configuration is shown in Fig. 30. It is “inverting” because our signal input comes to the “ $-$ ” input, and therefore has the opposite sign to the output. The negative feedback is provided by the resistor R_2 connecting output to input.

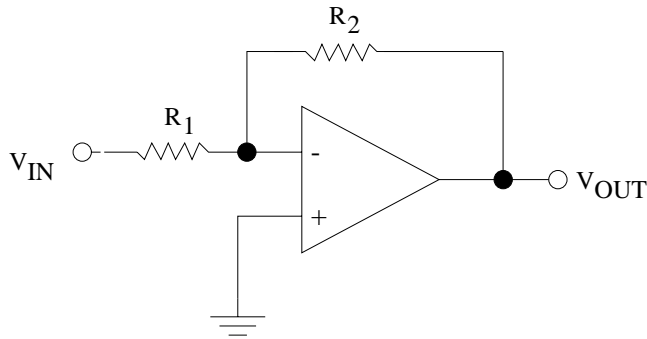


Figure 30: Inverting amplifier configuration.

We can use our rules to analyze this circuit. Since input $+$ is connected to ground, then by rule 1, input $-$ is also at ground. For this reason, the input $-$ is said to be at *virtual ground*. Therefore, the voltage drop across R_1 is $v_{\text{in}} - v_- = v_{\text{in}}$, and the voltage drop across R_2 is $v_{\text{out}} - v_- = v_{\text{out}}$. So, applying Kirchoff’s first law to the node at input $-$, we have, using golden rule 2:

$$i_- = 0 = i_{\text{in}} + i_{\text{out}} = v_{\text{in}}/R_1 + v_{\text{out}}/R_2$$

or

$$G = v_{\text{out}}/v_{\text{in}} = -R_2/R_1 \quad (34)$$

The input impedance, as always, is the impedance to ground for an input signal. Since the $-$ input is at (virtual) ground, then the input impedance is simply R_1 :

$$Z_{\text{in}} = R_1 \quad (35)$$

The output impedance is very small ($< 1 \Omega$), and we will discuss this again soon.

6.3 Non-inverting Amplifier

This configuration is given in Fig. 31. Again, its basic properties are easy to analyze in terms of the golden rules.

$$v_{\text{in}} = v_+ = v_- = v_{\text{out}} \left[\frac{R_1}{R_1 + R_2} \right]$$

where the last expression is from our voltage divider result. Therefore, rearranging gives

$$G = v_{\text{out}}/v_{\text{in}} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1} \quad (36)$$

The input impedance in this case is given by the intrinsic op-amp input impedance. As mentioned above, this is very large, and is typically in the following range:

$$Z_{\text{in}} \sim 10^8 \text{ to } 10^{12} \Omega \quad (37)$$

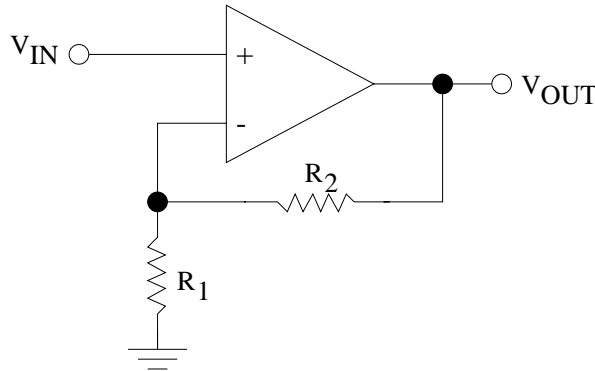


Figure 31: Non-inverting amplifier configuration.

6.4 Departures from Ideal

It is no surprise that the golden rules are not exact. On the other hand, they generally describe most, if not all, observed op-amp behavior. Here are some departures from ideal performance.

- *Offset voltage*, V_{OS} . Recall that the input of the op-amp is a differential pair. If the two transistors are not perfectly matched, an offset will show up as a non-zero DC offset at the output. As you found in Lab 4, this can be zeroed externally. This offset adjustment amounts to changing the ratio of currents coming from the emitters of the two input transistors.
- *Bias current*, I_{bias} . The transistor inputs actually do draw some current, regardless of golden rule 2. Those which use bipolar input transistors (*e.g.* the 741) draw more current than those which use FETs (*e.g.* the 411). The bias current is defined to be the average of the currents of the two inputs.
- *Offset current*, I_{OS} . This is the difference between the input bias currents. Each bias current, after passing through an input resistive network, will effectively offer a voltage to the op-amp input. Therefore, an offset of the two currents will show up as a voltage offset at the output.

Perhaps the best way to beat these effects, if they are a problem for a particular application, is to choose op-amps which have good specifications. For example, I_{OS} can be a problem for bi-polar designs, in which case choosing a design with FET inputs will usually solve the problem. However, if one has to deal with this, it is good to know what to do. Figure 32 shows how this might be accomplished. Without the $10\text{ k}\Omega$ resistors, this represents a non-inverting amplifier with voltage gain of $1 + (10^5/10^2) \approx 1000$. The modified design in the figure gives a DC path from ground to the op-amp inputs which are approximately equal in resistance ($10\text{ k}\Omega$), while maintaining the same gain.

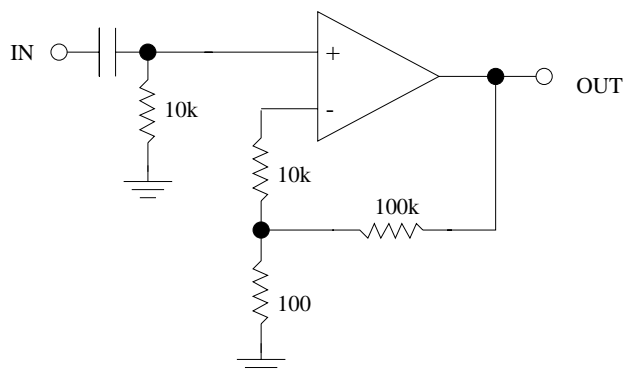


Figure 32: Non-inverting amplifier designed to minimize effect of I_{OS} .

Similarly, the inverting amplifier configuration can be modified to mitigate offset currents. In this case one would put a resistance from the $-$ input to ground which is balanced by the R_1 and R_2 in parallel (see Fig. 30).

It is important to note that, just as we found for transistor circuits, one should always *provide a DC path to ground for op-amp inputs*. Otherwise, charge will build up on the effective capacitance of the inputs and the large gain will convert this voltage ($= Q/C$) into a large and uncontrolled output voltage offset.

However, our modified designs to fight I_{OS} have made our op-amp designs worse in a general sense. For the non-inverting design, we have turned the very large input impedance into a not very spectacular $10\text{ k}\Omega$. In the inverting case, we have made the virtual ground into an approximation. One way around this, if one is concerned only with AC signals, is to place a capacitor in the feedback loop. For the non-inverting amplifier, this would go in series with the resistor R_1 to ground. Therefore, as stated before, it is best, where important, to simply choose better op-amps!

6.5 Frequency-dependent Feedback

Below are examples of simple integrator and differentiator circuits which result from making the feedback path have frequency dependence, in these cases single-capacitor RC filters. It is also possible to modify non-inverting configurations in a similar way. For example, problem (3) on page 251 of the text asks about adding a “rolloff” capacitor in this way. Again, one would simply modify our derivations of the basic inverting and non-inverting gain formulae by the replacements $R \rightarrow Z$, as necessary.

6.5.1 Integrator

Using the golden rules for the circuit of Fig. 33, we have

$$\frac{v_{\text{in}} - v_-}{R} = \frac{v_{\text{in}}}{R} = i_{\text{in}} = i_{\text{out}} = -C \frac{d(v_{\text{out}} - v_-)}{dt} = -C \frac{dv_{\text{out}}}{dt}$$

So, solving for the output gives

$$v_{\text{out}} = -\frac{1}{RC} \int v_{\text{in}} dt \quad (38)$$

And for a single Fourier component ω , this gives for the gain

$$G(\omega) = -\frac{1}{\omega RC} \quad (39)$$

Therefore, to the extent that the golden rules hold, this circuit represents an *ideal integrator* and a low-pass filter. Because of the presence of the op-amp, this is an example of an *active filter*. In practice, one may need to supply a resistor in parallel with the capacitor to give a DC path for the feedback.

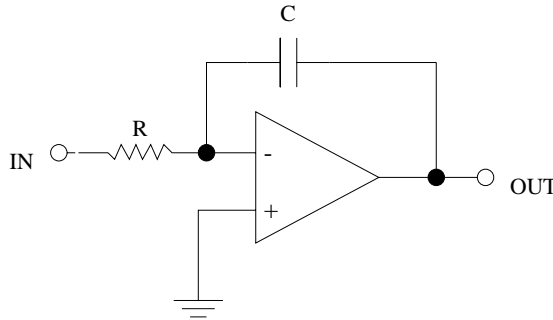


Figure 33: Op-amp integrator or low-pass filter.

6.5.2 Differentiator

The circuit of Fig. 34 can be analyzed in analogy to the integrator. We find the following:

$$v_{\text{out}} = -RC \frac{dv_{\text{in}}}{dt} \quad (40)$$

$$G(\omega) = -\omega RC \quad (41)$$

So this ideally represents a perfect differentiator and an active high-pass filter. In practice, one may need to provide a capacitor in parallel with the feedback resistor. (The gain cannot really increase with frequency indefinitely!)

6.6 Negative Feedback

As we mentioned above, the first of our Golden Rules for op-amps required the use of negative feedback. We illustrated this with the two basic negative feedback configurations: the inverting and the non-inverting configurations. In this section we will discuss negative feedback in a very general way, followed by some examples illustrating how negative feedback can be used to improve performance.

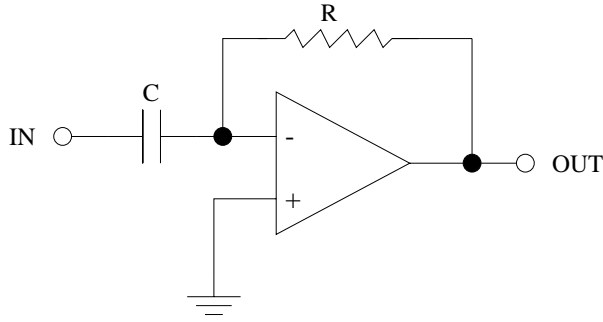


Figure 34: Op-amp differentiator or high-pass filter.

6.6.1 Gain

Consider the rather abstract schematic of a negative feedback amplifier system shown in Fig. 35. The symbol \otimes is meant to indicate that negative feedback is being added to the input. The op-amp device itself has intrinsic gain A . This is called the op-amp's *open-loop gain* since this is the gain the op-amp would have in the absence of the feedback loop. The quantity B is the fraction of the output which is fed back to the input. For example, for the non-inverting amplifier this is simply given by the feedback voltage divider: $B = R_1/(R_1 + R_2)$. The gain of the device is, as usual, $G = v_{\text{out}}/v_{\text{in}}$. G is often called the *closed-loop gain*. To complete the terminology, the product AB is called the *loop gain*.

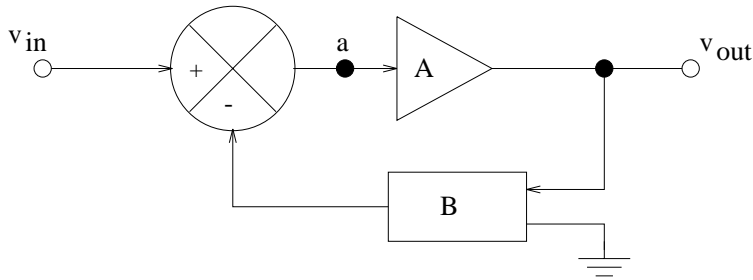


Figure 35: General negative feedback configuration.

As a result of the negative feedback, the voltage at the point labelled “a” in the figure is

$$v_a = v_{\text{in}} - Bv_{\text{out}}$$

The amplifier then applies its open-loop gain to this voltage to produce v_{out} :

$$v_{\text{out}} = Av_a = Av_{\text{in}} - ABv_{\text{out}}$$

Now we can solve for the closed-loop gain:

$$v_{\text{out}}/v_{\text{in}} \equiv G = \frac{A}{1 + AB} \quad (42)$$

Note that there is nothing in our derivation which precludes having B (or A) be a function of frequency.

6.6.2 Input and Output Impedance

We can now also calculate the effect that the closed-loop configuration has on the input and output impedance. The figure below is meant to clearly show the relationship between the definitions of input and output impedances and the other quantities of the circuit. The quantity R_i represents the open-loop input impedance of the op-amp, that is, the impedance the hardware had in the absence of any negative feedback loop. Similarly, R_o represents the Thevenin source (output) impedance of the open-loop device.

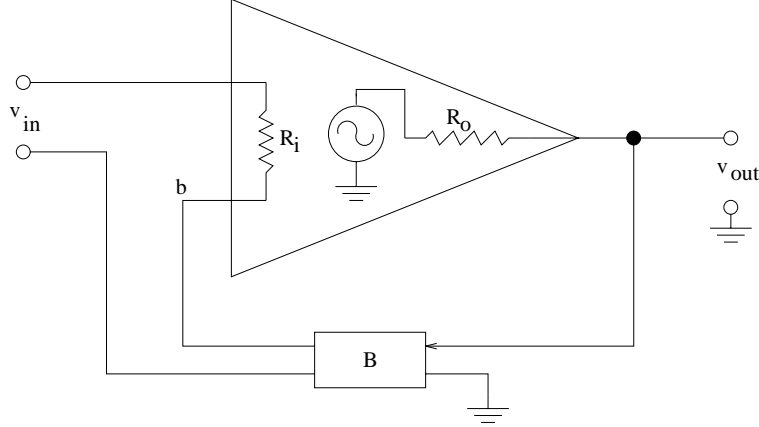


Figure 36: Schematic to illustrate the input and output impedance of a negative feedback configuration.

We start the calculation of Z_{in} with the definition $Z_{in} = v_{in}/i_{in}$. Let us calculate the current passing through R_i :

$$i_{in} = \frac{v_{in} - v_b}{R_i} = \frac{v_{in} - Bv_{out}}{R_i}$$

Substituting the result of Eqn. 42 gives

$$i_{in} = \frac{1}{R_i} \left[v_{in} - Bv_{in} \left(\frac{A}{1 + AB} \right) \right]$$

Rearranging allows one to obtain

$$Z_{in} = v_{in}/i_{in} = R_i [1 + AB] \quad (43)$$

A similar procedure allows the calculation of $Z_{out} \equiv v_{open}/i_{short}$. We have $v_{open} = v_{out}$ and the shorted current is what gets when the load has zero input impedance. This means that all of the current from the amplifier goes into the load, leaving none for the feedback loop. Hence, $B = 0$ and

$$i_{short} = A(v_{in} - Bv_{out})/R_o = Av_{in}/R_o = \frac{Av_{out}}{R_o G} = \left(\frac{Av_{out}}{R_o} \right) \left(\frac{1 + AB}{A} \right) = \frac{v_{out}}{R_o} (1 + AB)$$

This gives our result

$$Z_{out} = v_{open}/i_{short} = \frac{R_o}{1 + AB} \quad (44)$$

Therefore, the effect of the closed loop circuit is to improve both input and output impedances by the identical loop-gain factor $1 + AB \approx AB$. So for a typical op-amp like a 741 with $A = 10^3$, $R_i = 1 \text{ M}\Omega$, and $R_o = 100 \text{ }\Omega$, then if we have a loop with $B = 0.1$ we get $Z_{\text{in}} = 100 \text{ M}\Omega$ and $Z_{\text{out}} = 1 \text{ }\Omega$.

6.6.3 Examples of Negative Feedback Benefits

We just demonstrated that the input and output impedance of a device employing negative feedback are both improved by a factor $1 + AB \approx AB$, the device loop gain. Now we give a simple example of the gain equation Eqn. 42 in action.

An op-amp may typically have an open-loop gain A which varies by at least an order of magnitude over a useful range of frequency. Let $A_{\text{max}} = 10^4$ and $A_{\text{min}} = 10^3$, and let $B = 0.1$. We then calculate for the corresponding closed-loop gain extremes:

$$G_{\text{max}} = \frac{10^4}{1 + 10^3} \approx 10(1 - 10^{-3})$$

$$G_{\text{min}} = \frac{10^3}{1 + 10^2} \approx 10(1 - 10^{-2})$$

Hence, the factor of 10 open-loop gain variation has been reduced to a 1% variation. This is typical of negative feedback. It attenuates errors which appear within the feedback loop, either internal or external to the op-amp proper.

In general, the benefits of negative feedback go as the loop gain factor AB . For most op-amps, A is very large, starting at $> 10^5$ for $f < 100 \text{ Hz}$. A large gain G can be achieved with large A and relatively small B , at the expense of somewhat poorer performance relative to a smaller gain, large B choice, which will tend to very good stability and error compensation properties. An extreme example of the latter choice is the “op-amp follower” circuit, consisting of a non-inverting amplifier (see Fig. 31) with $R_2 = 0$ and R_1 removed. In this case, $B = 1$, giving $G = A/(1 + A) \approx 1$.

Another interesting feature of negative feedback is one we discussed briefly in class. The qualitative statement is that any signal irregularity which is put into the feedback loop will, in the limit $B \rightarrow 1$, be taken out of the output. This reasoning is as follows. Imagine a small, steady signal v_s , which is added within the feedback loop. This is returned to the output with the opposite sign after passing through the feedback loop. In the limit $B = 1$ the output and feedback are identical ($G = 1$) and the cancellation of v_s is complete. An example of this is that of placing a “push-pull” output stage to the op-amp output in order to boost output current. (See text Section 2.15.) The push-pull circuits, while boosting current, also exhibit “cross-over distortion”, as we discussed in class and in the text. However, when the stage is placed within the op-amp negative feedback loop, this distortion can essentially be removed, at least when the loop gain AB is large.

6.7 Compensation in Op-amps

Recall that an RC filter introduces a phase shift between 0 and $\pi/2$. If one cascades these filters, the phase shifts can accumulate, producing at some frequency ω_π the possibility of a phase shift of $\pm\pi$. This is dangerous for op-amp circuits employing negative feedback, as a phase shift of π converts negative feedback to *positive* feedback. This in turn tends to

compound circuit instabilities and can lead to oscillating circuits (as we do on purpose for the RC relaxation oscillator).

So it is perhaps easy to simply not include such phase shifts in the feedback loop. However, at high frequencies ($f \sim 1$ MHz or more), unintended stray capacitances can become significant. In fact, within the op-amp circuits themselves, this is almost impossible to eliminate. Most manufacturers of op-amps confront this issue by intentionally reducing the open-loop gain at high frequency. This is called *compensation*. It is carried out by bypassing one of the internal amplifier stages with a high-pass filter. The effect of this is illustrated in Fig. 37. It is a so-called “Bode plot”, $\log_{10}(A)$ vs $\log_{10}(f)$, showing how the intrinsic gain of a compensated op-amp (like the 741 or 411) decreases with frequency much sooner than one without compensation. The goal is to achieve $A < 1$ at ω_{π} , which is typically at frequencies of 5 to 10 MHz. (One other piece of terminology: The frequency at which the op-amp open-loop gain, A , is unity, is called f_T , and gives a good indication of how fast the op-amp is.

Compensation accounts for why op-amps are not very fast devices: The contribution of the higher frequency Fourier terms are intentionally attenuated. However, for comparators, which we turn to next, negative feedback is not used. Hence, their speed is typically much greater.

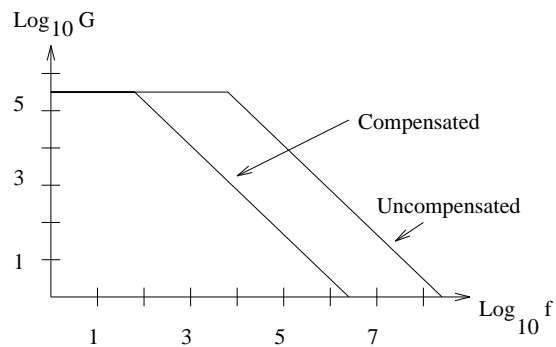


Figure 37: Bode plot showing effect of op-amp compensation.