

Homework #7, due Thursday March 9

1. Text 11.18
2. Text page 559:12
3. Repeat problem 3 of Homework #6 (the “vending machine”) using a ROM in place of logic gates for **present state** \rightarrow **next state**. Indicate how much memory is required in $m \times n$ notation, and assign a value to each of these bits.